
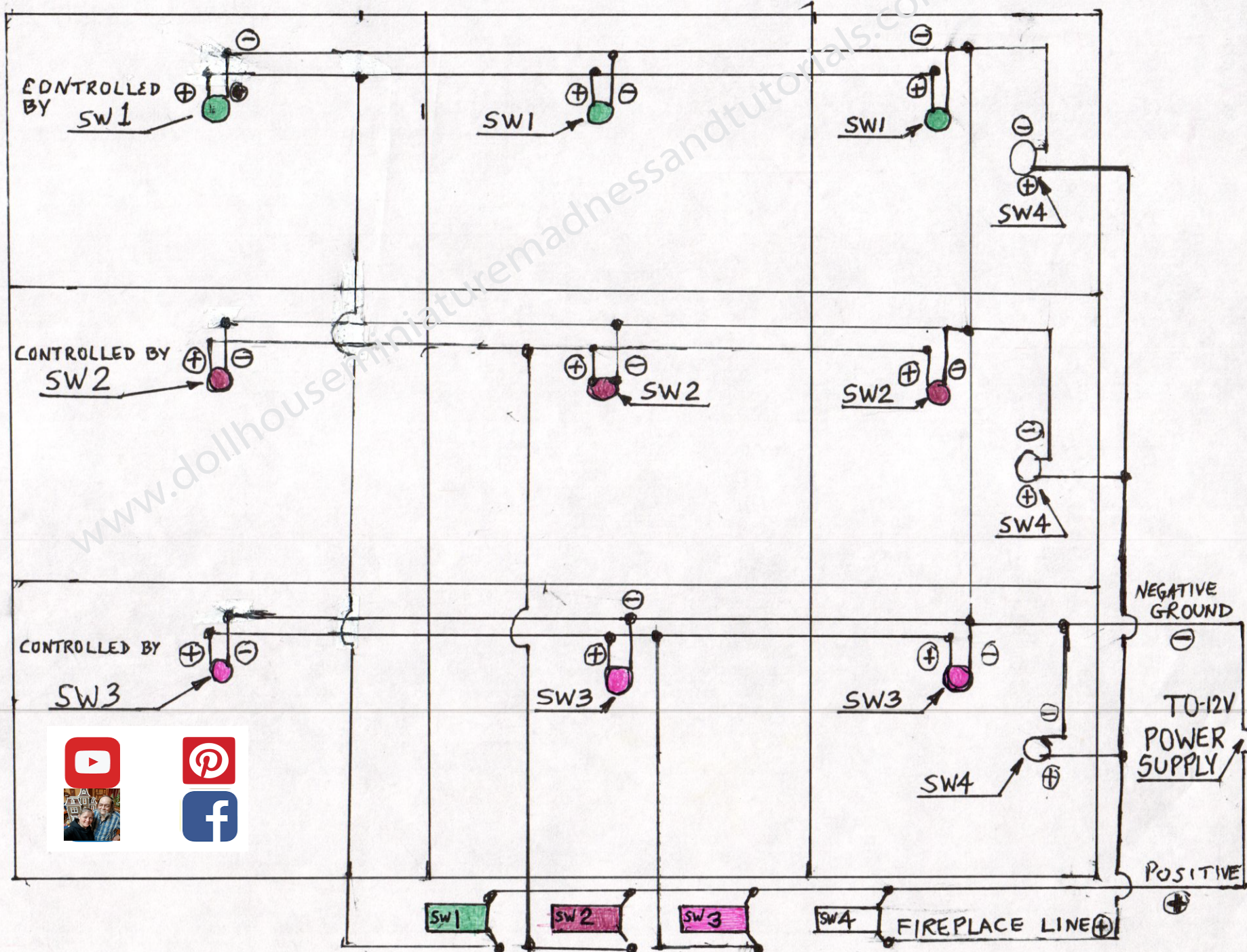


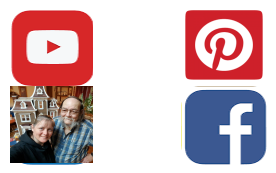
# HOW TO WIRE EACH FLOOR ON SEPARATE SWITCHES FOR 12VOLT LED'S



<http://www.dollhouseminiaturemadnessandtutorials.com>



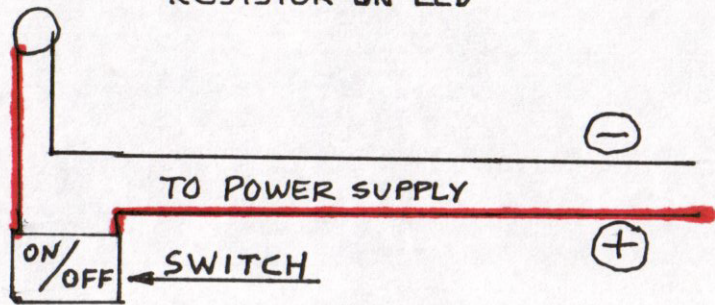HOW TO WIRE ONE LED WITH  
RESISTOR ON LED



MORE THAN ONE LED ON SWITCH

